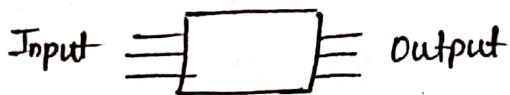


## Combinational circuit and Sequential circuit

### Digital electronics

↓  
Combinational circuit  
output is only depending  
on present input




→ No feedback

→ No memory

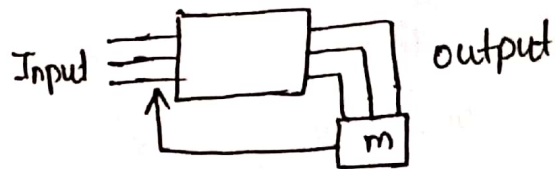Example: • Half Adder, Full Adder


- Half Subtractor, Full Subtractor
- Multiplexer and Demultiplexer
- Decoder, Encoder
- Code converter

↓  
Sequential circuit  
output is depending on present  
input and past output



Example: • Counter  
• Shift register  
• Flip Flop

## Designing of combinational circuits:

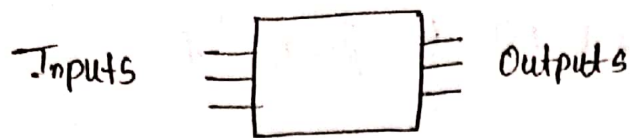

Step-1: Determine and define total inputs and outputs of the circuit.

Step-2: Make truth table that defines relationship in between inputs and outputs.

Step-3: Determine boolean equation using k-map.

Step-4: Based on boolean equation we can form circuit.

Question: 01

The minimal function that can detect "divisible by 2" with 8421 BCD  $[D_8 D_4 D_2 D_1]$  is given by \_\_\_\_\_


	$D_8$	$D_4$	$D_2$	$D_1$	$Y$
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	X
11	1	0	1	1	X
12	1	1	0	0	X
13	1	1	0	1	X
14	1	1	1	0	X
15	1	1	1	1	X

$D_8 D_4$	$\overline{D_8} \overline{D_4}$	$\overline{D_8} D_4$	$D_8 \overline{D_4}$	$D_8 D_4$
$D_2 D_1$	00	01	11	10
$D_2 D_1, 00$	1	1	X	1
$\overline{D_2} D_1, 01$	0	0	X	0
$D_2 \overline{D_1}, 11$	0	0	X	X
$D_2 D_1, 10$	1	1	X	X

$$Y = \overline{D_1}$$

Question-2 The minimal function that can detect "divisible by 3" with 8421 BCD  $[D_8 D_4 D_2 D_1]$  is given by —

	$D_8$	$D_4$	$D_2$	$D_1$	$y$
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	1
10	1	0	1	0	x
11	1	0	1	1	x
12	1	1	0	0	x
13	1	1	0	1	x
14	1	1	1	0	x
15	1	1	1	1	x

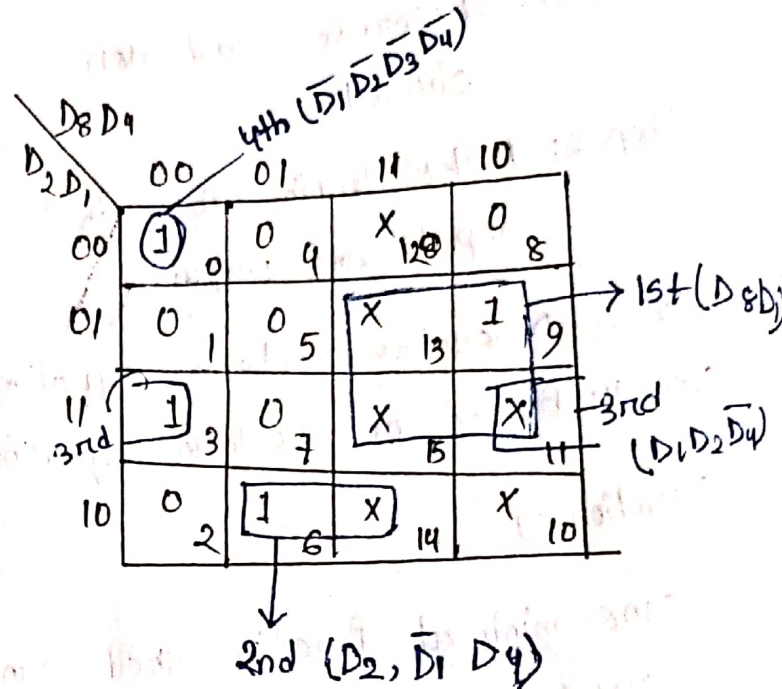


$$y = D_1 D_8 + \bar{D}_1 D_2 D_4 + D_1 D_2 \bar{D}_4 + \bar{D}_1 \bar{D}_2 \bar{D}_3 \bar{D}_4$$






## Half Adder


→ we perform two bit addition

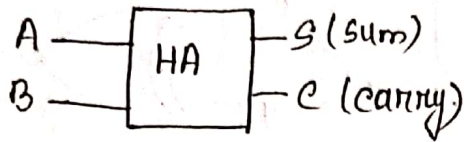

A	B	S	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

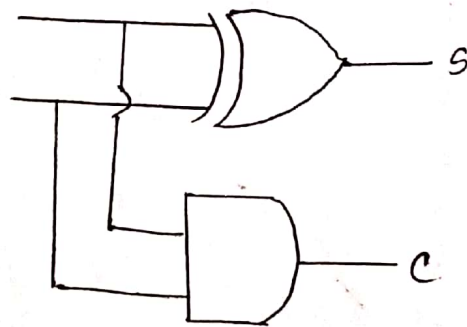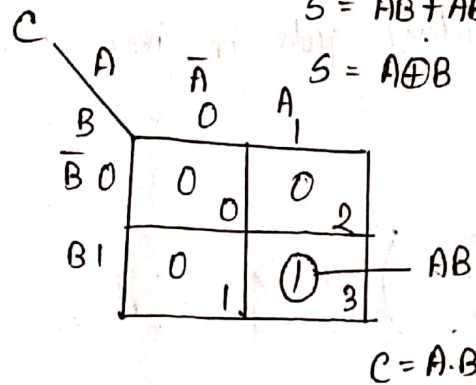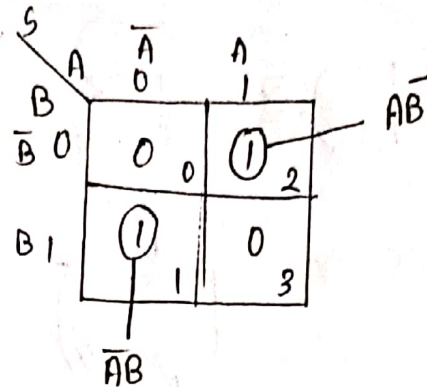

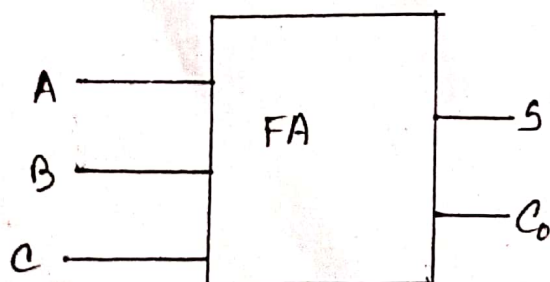Full Adder: used to perform 3 bit addition



	A	B	C	S	C <sub>0</sub>
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

		AB	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$	$\bar{A}\bar{B}$
C	0	00	01	10	11	00	01
	1	01	10	11	00	10	11

		$\bar{A}\bar{B}C$	$\bar{A}B\bar{C}$	$A\bar{B}C$	$AB\bar{C}$
0	0	0	0	0	0
1	0	0	1	0	0
2	0	1	0	0	0
3	0	1	1	0	0
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1


$$\begin{aligned}
 S &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C + AB\bar{C} \\
 &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}C + B\bar{C}) \\
 &= \bar{A}(B \oplus C) + A(B \oplus C) \\
 &= \bar{A}(B \oplus C) + A(B \oplus C)
 \end{aligned}$$

		AB	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$	$\bar{A}\bar{B}$
C	0	00	01	10	11	00	01
	1	01	10	11	00	10	11


  

		$BC$	$AB$	$AC$
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

$$C_0 = AB + BC + AC$$

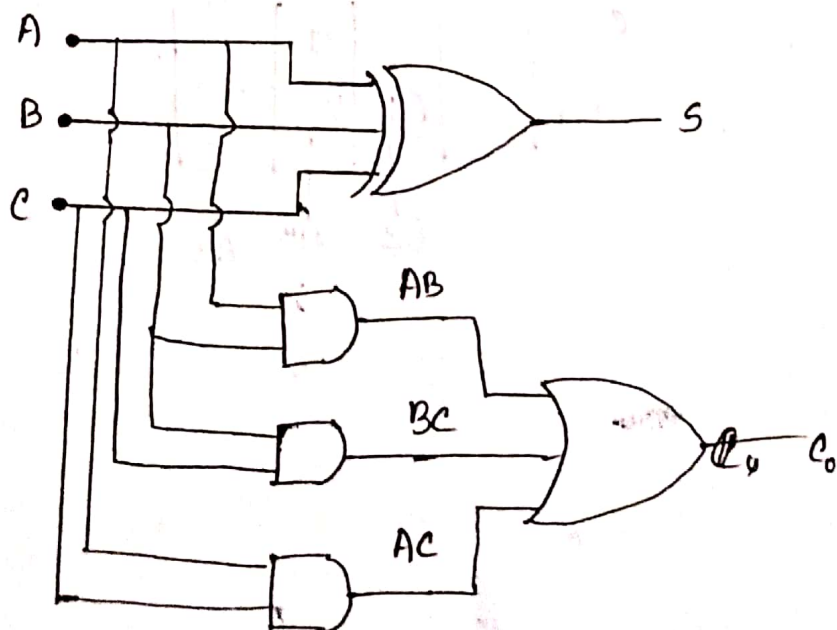


## Full Adder circuit using half Adder

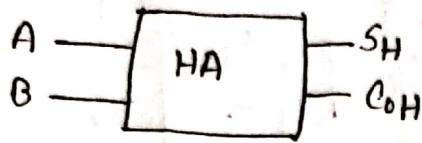


$$S_H = A \oplus B$$

$$C_{0H} = A \cdot B$$

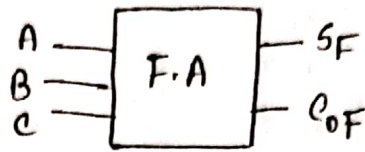

$$S_F = A \oplus B \oplus C$$

$$S_{0F} = AB + BC + CA$$

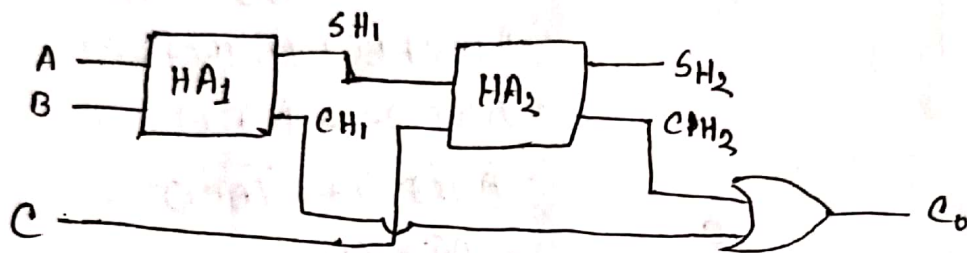

$$S_{H1} = A \oplus B$$

$$= \bar{A}\bar{B} + \bar{A}B$$

$$C_{H1} = A \cdot B$$

$$S_{H2} = S_{H1} \oplus C = A \oplus B \oplus C$$

$$C_{H2} = S_{H1} \cdot C$$

$$= (\bar{A}\bar{B} + \bar{A}B) \cdot C$$

$$= \bar{A}\bar{B}C + \bar{A}BC$$

$$C_0 = C_{H1} + C_{H2}$$

$$= AB + \bar{A}\bar{B}C + \bar{A}BC$$



$C_0$

		$C$			
		$\bar{C}$	$C$	$\bar{C}$	$C$
$A$	$B$	0	1	0	1
		0	0	0	0
0	1	0	1	0	1
1	0	0	1	1	0
1	1	1	0	1	1



Groupings for  $C_0$  (Carry Out):

- Group 1:  $\bar{A}\bar{B}C$  (Cells:  $(A=0, B=0, C=1)$  and  $(A=0, B=1, C=1)$ )
- Group 2:  $\bar{A}BC$  (Cells:  $(A=0, B=1, C=1)$  and  $(A=1, B=1, C=1)$ )
- Group 3:  $AB$  (Cells:  $(A=1, B=0, C=1)$  and  $(A=1, B=1, C=1)$ )

## HALF ADDER BY NAND GATES

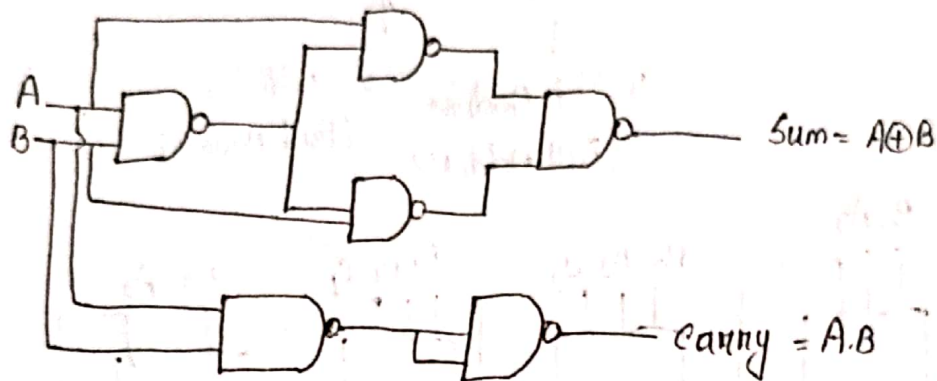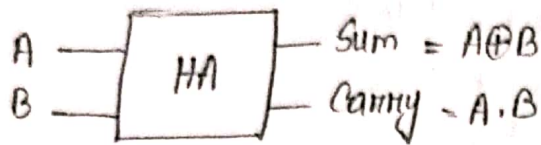

## HALF ADDER BY NOR GATES

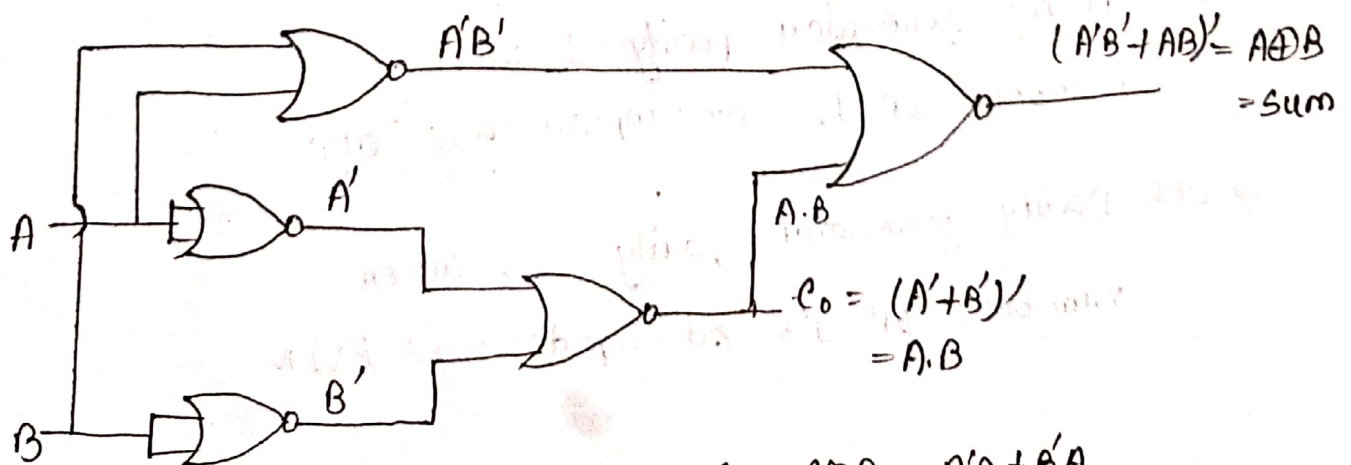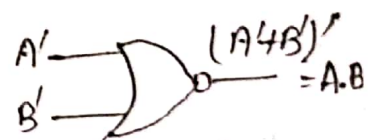

$$S = A \oplus B = A'B + B'A$$

$$= \overline{(A'B' + AB)}$$




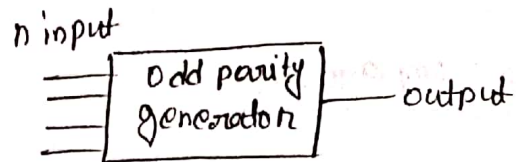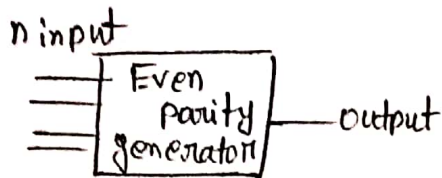
## Even parity Generator / odd parity Generator

⇒ Even parity generator parity = 1 when numbers of 1's at inputs are ODD

⇒ ODD parity generator parity = 1, when numbers of 1's at inputs are EVEN.





	$b_3$	$b_2$	$b_1$	$b_0$	O/P (Even parity) $P$	O/P (Odd parity) $Q$
(0)	0	0	0	0	0	1
(1)	0	0	0	1	1	0
(2)	0	0	1	0	1	0
(3)	0	0	1	1	0	1
(4)	0	1	0	0	1	0
(5)	0	1	0	1	0	1
(6)	0	1	1	0	0	1
(7)	0	1	1	1	1	0
(8)	1	0	0	0	1	0
(9)	1	0	0	1	0	1
(10)	1	0	1	0	1	0
(11)	1	0	1	1	1	0
(12)	1	1	0	0	0	1
(13)	1	1	0	1	1	0
(14)	1	1	1	0	1	0
(15)	1	1	1	1	0	1


$P$

$b_3 b_2$	00	01	11	10
00	0 <sub>0</sub>	1 <sub>4</sub>	0 <sub>12</sub>	1 <sub>8</sub>
01	1 <sub>1</sub>	0 <sub>5</sub>	1 <sub>13</sub>	0 <sub>9</sub>
11	0 <sub>3</sub>	1 <sub>7</sub>	0 <sub>15</sub>	1 <sub>11</sub>
10	1 <sub>2</sub>	0 <sub>6</sub>	1 <sub>14</sub>	0 <sub>10</sub>

$$Q = \overline{b_3 \oplus b_1 \oplus b_2 \oplus b_0}$$

$$P(b_0, b_1, b_2, b_3) = b_0 \oplus b_1 \oplus b_2 \oplus b_3$$

## 2 bits comparator

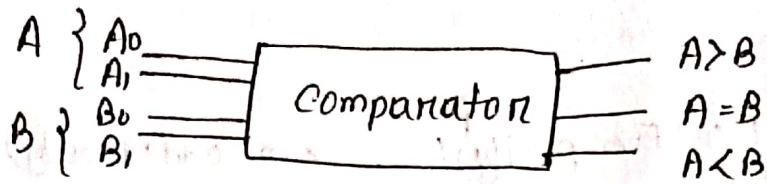

A <sub>1</sub>	A <sub>0</sub>	B <sub>1</sub>	B <sub>0</sub>	A > B	A = B	A < B	
0	0	0	0	0	1	0	0
0	0	0	1	0	0	1	1
0	0	1	0	0	0	1	2
0	0	1	1	0	0	1	3
0	1	0	0	1	0	0	4
0	1	0	1	0	1	0	5
0	1	1	0	0	0	1	6
0	1	1	1	0	0	1	7
1	0	0	0	1	0	0	8
1	0	0	1	1	0	0	9
1	0	1	0	0	1	0	10
1	0	1	1	0	0	1	11
1	1	0	0	1	0	0	12
1	1	0	1	1	0	0	13
1	1	1	0	1	0	0	14
1	1	1	1	0	1	0	15

$(A > B)$

$B_1 B_0$	$A_1 A_0$ 00	$\bar{A}_1 \bar{A}_0$ 01	$\bar{A}_1 A_0$ 11	$A_1 \bar{A}_0$ 10
$\bar{B}_1 \bar{B}_0$ 00	0	1	1	1
$\bar{B}_1 B_0$ 01	0	0	1	1
$B_1 B_0$ 11	0	0	0	0
$B_1 \bar{B}_0$ 10	0	0	1	0

Annotations for  $(A > B)$ :

- 1st group:  $A_1 \bar{B}_1$  (points to cells 4, 5, 13, 9)
- 2nd group:  $A_0 \bar{B}_1 \bar{B}_0$  (points to cell 8)
- 3rd group:  $A_1 A_0 \bar{B}_0$  (points to cells 11, 13, 14)

$$(A > B) = A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0$$

$$= A_1 \bar{B}_1 + A_0 \bar{B}_0 (\bar{B}_1 + A_1)$$

$A = B$

$B_1 B_0$	$A_1 A_0$ 00	$\bar{A}_1 \bar{A}_0$ 01	$\bar{A}_1 A_0$ 11	$A_1 \bar{A}_0$ 10
$\bar{B}_1 \bar{B}_0$ 00	1	0	0	0
$\bar{B}_1 B_0$ 01	0	1	0	0
$B_1 B_0$ 11	0	0	1	0
$B_1 \bar{B}_0$ 10	0	0	0	1

Annotations for  $A = B$ :

- 1st group:  $\bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0$  (points to cell 0)
- 2nd group:  $\bar{A}_1 A_0 \bar{B}_1 B_0$  (points to cell 5)
- 3rd group:  $A_1 A_0 B_1 B_0$  (points to cell 15)
- 4th group:  $A_1 \bar{A}_0 B_1 \bar{B}_0$  (points to cell 10)

$$(A = B) = \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0 + A_1 A_0 B_1 B_0 + A_1 \bar{A}_0 B_1 \bar{B}_0$$

$$= \bar{A}_1 \bar{B}_1 (\bar{A}_0 \bar{B}_0 + A_0 B_0) + A_1 B_1 (B_1 B_0 + \bar{A}_0 \bar{B}_0)$$

$(A < B)$

$B_1 B_0$	$A_1 A_0$ 00	$\bar{A}_1 \bar{A}_0$ 01	$\bar{A}_1 A_0$ 11	$A_1 \bar{A}_0$ 10
$\bar{B}_1 \bar{B}_0$ 00	0	0	0	0
$\bar{B}_1 B_0$ 01	1	0	0	0
$B_1 B_0$ 11	1	1	0	1
$B_1 \bar{B}_0$ 10	1	1	0	0

Annotations for  $(A < B)$ :

- 1st group:  $\bar{A}_1 \bar{B}_1$  (points to cells 1, 3, 2, 6)
- 2nd group:  $\bar{A}_1 \bar{A}_0 B_0$  (points to cell 5)
- 3rd group:  $\bar{A}_0 B_1 B_0$  (points to cells 11, 10)

$$(A < B) = \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$$



