

## Flip Flop

1. What is flip flop
- ✓ 2. Truth table, characteristic table and excitation table of flip flop
- ✓ 3. SR Flip Flop
- ✓ 4. D Flip Flop
- ✓ 5. JK Flip Flop
- ✓ 6. T Flip Flop
- ✓ 7. Preset and clear inputs in Flip Flops
- ✓ 8. SR flip flop to D flip flop conversion
- ✓ 9. SR flip flop to JK flip flop conversion
- ✓ 10. SR flip flop to T flip flop conversion
- ✓ 11. JK flip flop to D flip flop conversion
- ✓ 12. JK flip flop to T flip flop conversion
- ✓ 13. D Flip flop to T flip flop . conversion
- ✓ 14. D Flip flop to JK flip flop . conversion


15. T flip flop to D flip flop conversion
16. T flip flop to JK flip flop conversion
17. JK flip flop to SR flip flop conversion, D flip flop to SR flip flop conversion and T flip flop to SR flip flop conversion
18. Examples on flip flops.

Q What is flip flop?

→ A flip flop is a sequential ~~circuit~~ digital electronic circuit having two stable states that can be used to store one bit of binary data.

## Truth table, characteristics table and Excitation table

### of Flip Flop:-

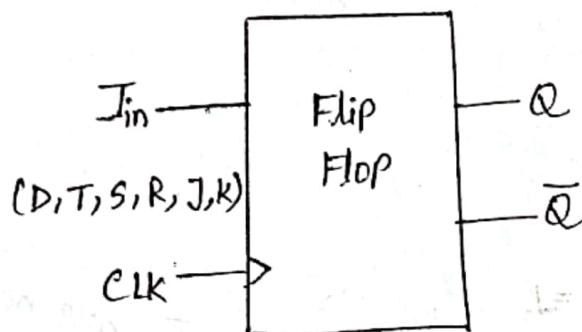

- \* D FF  $\rightarrow$   $J_{in}$  এর পরিযাত D
- T FF  $\rightarrow$   $J_{in}$  এর পরিযাত T
- SR FF  $\rightarrow$   $J_{in}$  এর পরিযাত S and R
- JK FF  $\rightarrow$   $J_{in}$  এর পরিযাত J and K

### Truth table:-

Inputs respect to outputs /Next state

CLK	$J_{in}$	$Q$	$\bar{Q}$	CLK	$J_{in}$	$Q_{n+1}$
-----	----------	-----	-----------	-----	----------	-----------

### Characteristics Table:-

Current state and Inputs respect to next state (output)

$Q_n$

$J_{in}$

$Q_{n+1}$

$Q_n$	$J_{in}$	$Q_{n+1}$
-------	----------	-----------

### Excitation Table:

Current state and Next state w.r.t. to inputs

$Q_n$


$Q_{n+1}$

$J_{in}$

$Q_n$	$Q_{n+1}$	$J_{in}$
-------	-----------	----------

SR flip flop:- SR flip flop is a gated set reset flip-flop.

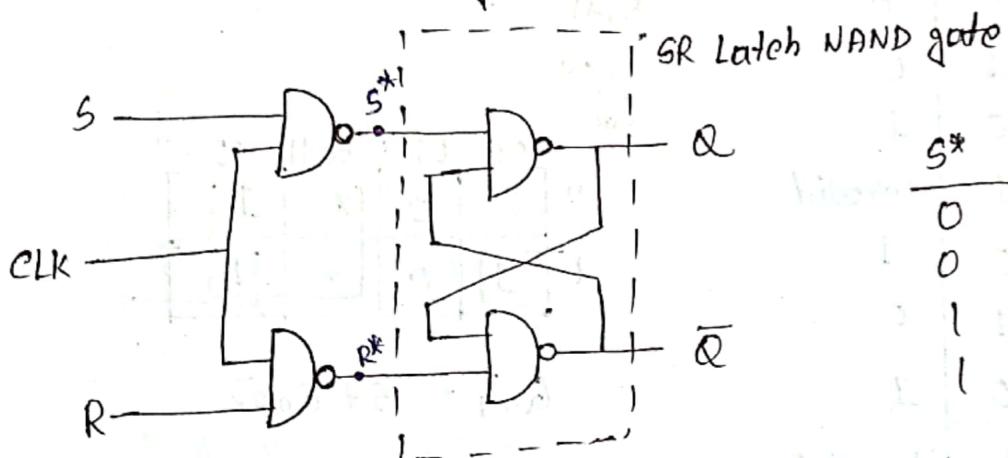The S and R inputs control the state of the flip flop when the clock pulse goes from Low to high.



S*	R*	Q	Q̄
0	0	Invalid	
0	1	1	0
1	0	0	1
1	1	Memory	

$$\text{Hence, } S^* = \overline{S \cdot \text{CLK}} = \overline{S} + \overline{\text{CLK}}$$

$$R^* = \overline{R \cdot \text{CLK}} = \overline{R} + \overline{\text{CLK}}$$

when,  $\text{CLK} = 1$

$$S^* = \overline{S} \text{ and } R^* = \overline{R}$$

For nand gate  
input=0 then  
output=1

Truth Table:

CLK	S	R	Q	Q̄
0	x	x	Memory	
1	0	0	Memory	
1	0	1	0	1
1	1	0	1	0
1	1	1	Invalid	

CLK	S	R	Q <sub>n+1</sub>
0	x	x	Q <sub>n</sub>
1	0	0	Q <sub>n</sub>
1	0	1	0
1	1	0	1
1	1	1	Invalid

## Characteristic Table:

$Q_n$	$S$	$R$	$Q_{n+1}$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	Invalid
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	Invalid

$Q_n$   
SR

	00	01	10	11
0	0	0	X	1
1	1	0	X	1



$$Q_{n+1} = S + Q_n \cdot R$$

## Excitation Table:

$Q_n$	$Q_{n+1}$	$S$	$R$
0	0	0	X
0	1	1	0
1	0	0	1
1	1	1	0

0	0	0	0	0
0	0	0	X	0
0	1	0	0	1
1	0	0	1	0
1	1	0	1	1

## D Flip Flop (Data-Flip-flop)

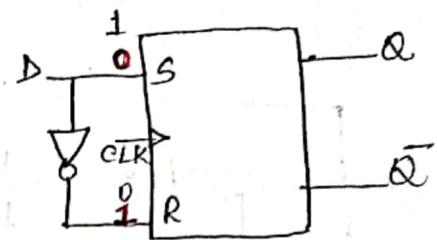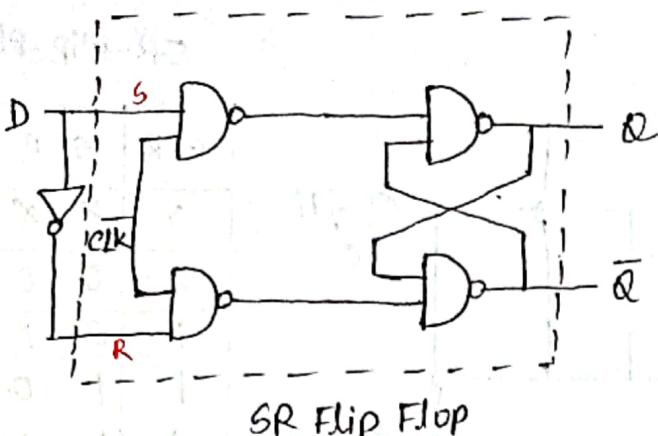

As per data flip-flop  
Input will get transferred  
to output in next state.

Truth table:

CLK	S	R	$Q_{n+1}$
0	X	X	$Q_n$
1	0	0	$Q_n$
1	0	1	0
1	1	0	1
1	1	1	Invalid

CLK	D	$Q_{n+1}$
0	X	$Q_n$
1	0	0
1	1	1

Characteristic Table:


$Q_n$	D	$Q_{n+1}$
0	0	0
0	1	1
1	0	0
1	1	1

$$Q_{n+1} = D$$

Excitation table:

$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

## Jk flip flop:

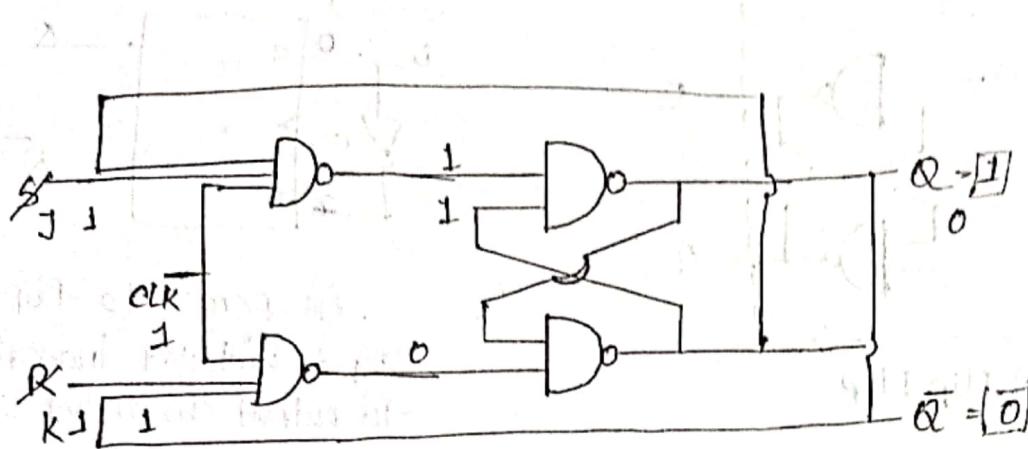

SR - flip - flop - truth - table

CLK	S	R	$Q \bar{Q}$
0	x	x	memory
1	0	0	memory
1	0	1	0 1
1	1	0	1 0
1	1	1	Invalid

J-K flip flop - truth - table:

CLK	J	K	Q	$\bar{Q}$
0	x	x	Memory	
1	0	0	Memory	
1	0	1	0	1
1	1	0	1	0
1	1	1	Memory	

/ Truth-table

CLK	J	K	$Q_{n+1}$
0	x	x	$Q_n$
1	0	0	$Q_n$
1	0	1	0
1	1	0	1
1	1	1	$\bar{Q}_n$

$Q = 1$  and  $\bar{Q} = 0$ ,  
 $CLK = 1$ ,  $J = 1$ ,  $K = 1$ ;  $Q = 0$  and  $\bar{Q} = 1$

JK characteristic - table

	$Q_n$	J	K	$Q_{n+1}$
0	0	0	0	0
2	0	0	1	0
4	0	1	0	1
6	0	1	1	1
1	1	0	0	1
3	1	0	1	0
5	1	1	0	1
7	1	1	1	0

$Q_{n+1}$	1	1	0	0	1
$Q_n$	0	0	0	1	1
$J$	00	01	11	10	JK
0	0	0	1	1	
1	1	0	0	0	1

$$Q_{n+1} = \bar{Q}_n J + Q_n \bar{K}$$

## Excitation table



$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$Q_n$	$Q_{n+1}$	J	K	$Q_n$	$Q_{n+1}$
0	0	0	1	0	1
1	X <sub>1</sub>	X <sub>2</sub>	1	1	0

$$J = Q_n + \bar{J} \quad K = \overline{Q_{n+1}}$$
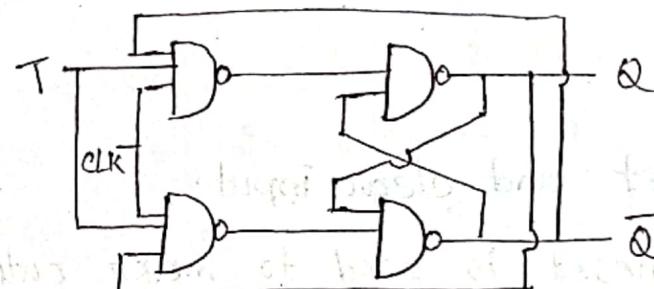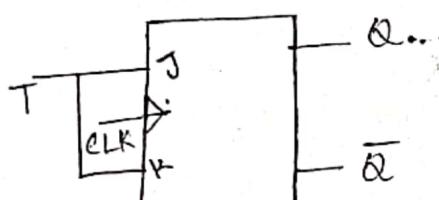
## T Flip Flop (Toggle flip flop)

Output will toggle (change) with respect to input along with clock signal.



## Truth table of JK Flip Flop

CLK	J	K	Q	$\bar{Q}$
0	X	X	Memory	
1	0	0	Memory	
1	0	1	0	1
1	1	0	1	0
1	1	1	Memory	

## Truth table of D Flip Flop

CLK	T	Q	$\bar{Q}$
0	X	Memory	
1	0	Memory	
1	1	Memory	

CLK	T	$Q_{n+1}$
0	X	$Q_n$
1	0	$Q_n$
1	1	$\bar{Q}_n$

## Characteristics - table:

$Q_n$	$T$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

Excitation table

$Q_n$	$Q_{n+1}$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

$$Q_{n+1} = \bar{Q}_n T + Q_n \bar{T}$$

$$= Q_n \oplus T$$


$$T = \bar{Q}_n Q_{n+1} + Q_n \bar{Q}_{n+1}$$

$$\Rightarrow Q_n \oplus Q_{n+1}$$

## Preset and clear input:

1. Preset is used to make output  $Q=1$
2. clear input is used to make output  $Q=0$
3. Preset and clear input doesn't need synchronization.
4. It gives a predefined output without bothering other inputs.

For nand, input=0 ; output=1

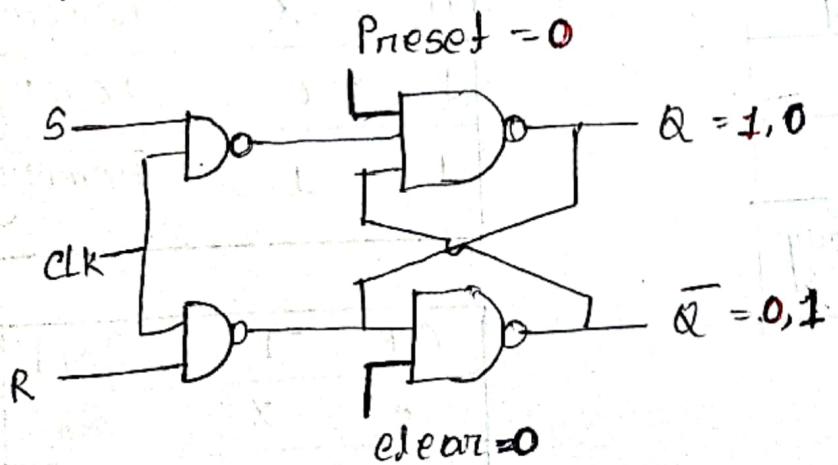

Preset = 0


$Q = 1, \bar{Q} = 0$

clear = 0

$\bar{Q} = 1, Q = 0$

Truth table :

Preset	clear	$Q_n$
0	0	Not used
0	1	1
1	0	0
1	1	FF operation

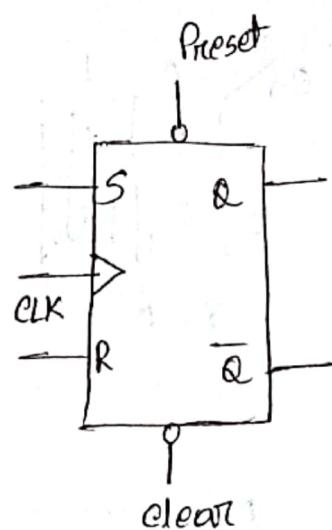

### SR to D Flip Flop conversion:

- Steps:
  - ① Note available flip flop and required -flip flop
  - ② Write characteristic table of required FF
  - ③ Write Excitation table of available FF
  - ④ Solve boolean expression
  - ⑤ Draw circuit

Hence, Available Flip Flop  $\rightarrow$  SR FF

Required Flip Flop  $\rightarrow$  D FF

characteristic table of required FF(DFF)

Excitation table (SR)


$Q_n$	D	$Q_{n+1}$	S	R
0	0	0	0	X
0	1	1	1	0
1	0	0	0	1
1	1	1	X	0

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

$S$	$D$	$Q_n$	$Q_{n+1}$	$S$	$R$	$D$	$Q_n$	$Q_{n+1}$
0	0	0	1	0	0	X	0	0
1	0	1	X	1	1	0	1	0

$$S = D$$

$$R = \bar{D}$$

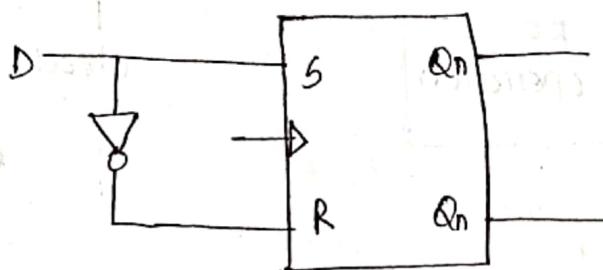

### SR to JK flip-flop conversion:

- ① Note available FF and required FF
- ② characteristic table of required FF
- ③ Write excitation table of available FFs
- ④ Solve Boolean expression
- ⑤ Draw circuit

Available Flip-flop = SR FF

Required Flip-flop = JK FF

characteristic table of JK FF

$JK$	$Q_n$	$J$	$K$	$Q_{n+1}$	$S$	$R$
0	0	0	0	0	0	X
2	0	0	1	0	0	X
4	0	1	0	1	1	0
6	0	1	1	1	1	0
1	1	0	0	1	X	0
3	1	0	1	0	0	1
5	1	1	0	1	X	0
7	1	1	1	0	0	-1

$Q_n$	$J$	$K$	$Q_{n+1}$	$S$	$R$
0	1	1	1	1	1
1	0	1	0	0	1
2	1	0	1	1	0
3	0	0	0	0	0
4	1	1	0	1	0
5	0	1	1	0	1
6	1	0	0	1	0
7	1	1	1	1	1

characteristic table of SR  
and JK FF

Excitation Table

## Excitation table of SR FF

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

JK


$Q_n$	00	01	11	10
0	0 <sub>0</sub>	0 <sub>2</sub>	1 <sub>6</sub>	1 <sub>4</sub>
1	X <sub>1</sub>	0 <sub>3</sub>	0 <sub>7</sub>	X <sub>5</sub>

$$S = \bar{Q}_n J$$

JK

$Q_n$	00	01	11	10
0	X <sub>0</sub>	X <sub>2</sub>	0 <sub>6</sub>	0 <sub>4</sub>
1	0 <sub>1</sub>	1 <sub>3</sub>	1 <sub>7</sub>	0 <sub>5</sub>

$$R = Q_n k$$

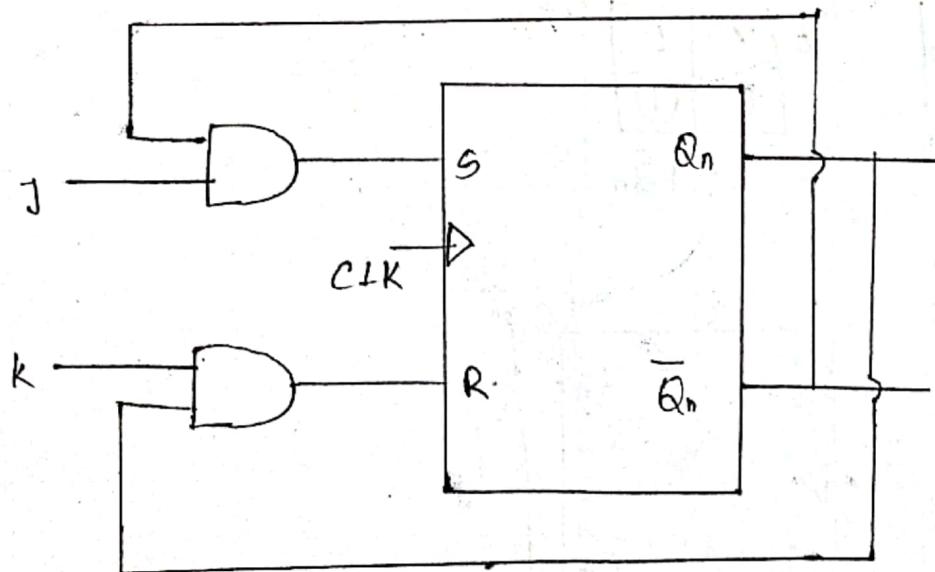

## SR to T flip flop conversion :

- ① Note available FF and required FF
- ② Write characteristics table of required FF
- ③ Write excitation table of available FF
- ④ Solve Boolean expression
- ⑤ Draw circuit.

Hence, Available FF = SR FF

Required FF = T FF

Characteristics table of T FF


$Q_n$	T	$Q_{n+1}$	S	R
0	0	0	0	X
0	1	1	X	0
1	0	1	X	0
1	1	0	0	1

Excitation table of SR FF

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

$$\begin{array}{c}
 \begin{array}{c}
 \begin{array}{c}
 \begin{array}{c}
 S \quad T \\
 \diagdown \quad \diagup \\
 Q_n \quad 0 \quad 1 \\
 \begin{array}{|c|c|c|} \hline & 0 & 0 \\ \hline & X & 1 \\ \hline \end{array} \quad \begin{array}{|c|c|c|} \hline & 1 & 0 \\ \hline & 0 & 1 \\ \hline \end{array} \\
 \end{array} \\
 \end{array} \\
 R \quad T \\
 \diagup \quad \diagdown \\
 Q_n \quad 0 \quad 1 \\
 \begin{array}{|c|c|c|} \hline & 0 & X \\ \hline & 1 & 0 \\ \hline \end{array} \quad \begin{array}{|c|c|c|} \hline & 0 & 1 \\ \hline & 1 & 0 \\ \hline \end{array} \\
 \end{array} \\
 \end{array}$$

$$S = T \bar{Q}_n \quad R = T Q_n$$

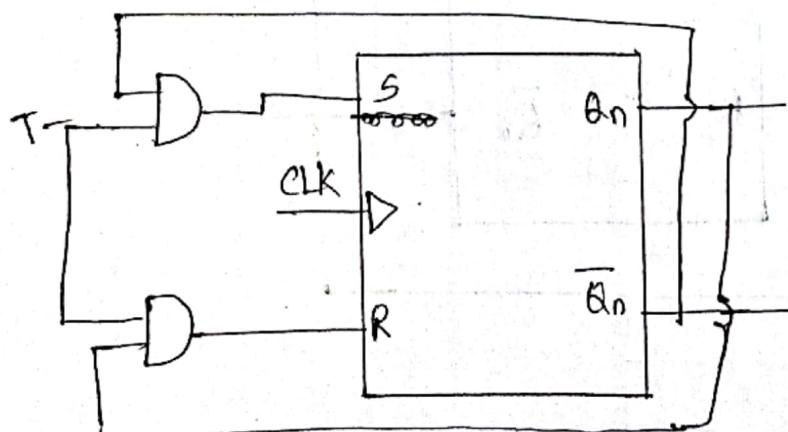

## Jk to D Flip Flop Conversion:


Steps - Same as previous conversions.

Here, Available FF = JK FF


Required FF = D FF

Characteristic Table of D FF

$Q_n$	D	$Q_{n+1}$	J	K
0	0	0	0	X
0	1	1	1	X
1	0	0	X	1
1	1	1	X	0

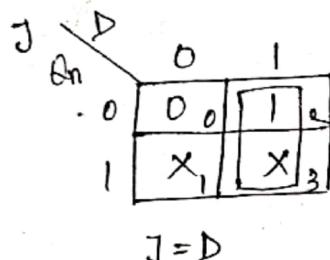


$$J = D$$

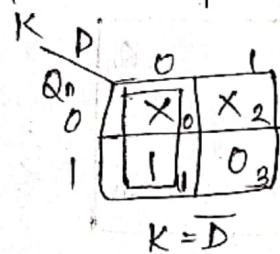

Excitation Table of JK FF

$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

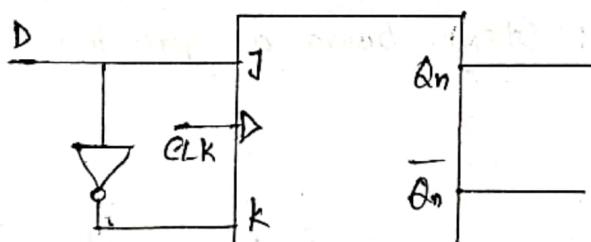

JK to T Flip Flop conversion: Steps - same as previous conversions

Here, Available Flip Flop = JK FF

Required Flip Flop = T FF

Characteristic table - T FF

Excitation table of JK FF

$Q_n$	T	$Q_{n+1}$	J	K
0	0	0	0	X
0	1	1	1	X
1	0	1	X	0
1	1	0	X	1

$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$J \searrow T \nearrow Q_n$


0	1
0	0 1 2
1	X 1 X 3

$$J = T$$

$K \searrow T \nearrow Q_n$

0	1
0	X 0 X 2
1	0 1 3

$$K = T$$

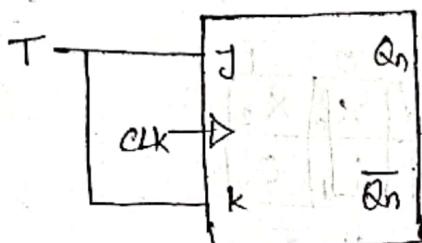

D to T flip-flop conversion: Steps: Same as previous conversion.

Available FF = D FF

Required FF = T FF

Characteristic table of T FF

$Q_n$	T	$Q_{n+1}$	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

$P \nearrow T \searrow Q_n$


0	1
0	0 1 2
1	1 0 3

Excitation table of D FF

$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

$Q_{n+1} \rightarrow D$
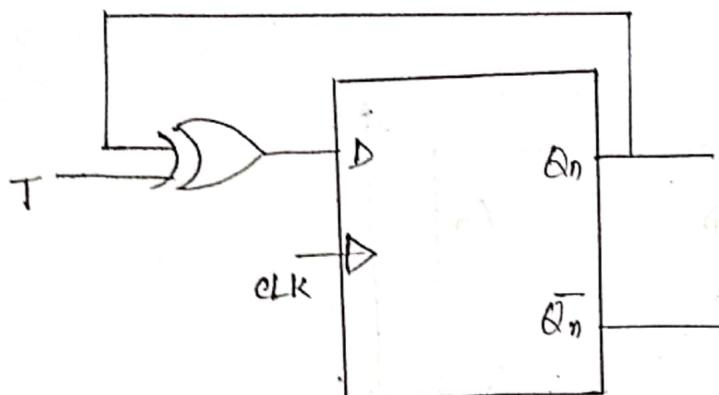
$$\begin{aligned} D &= T\bar{Q}_n + \bar{T}Q_n \\ &\Rightarrow T \oplus Q_n \end{aligned}$$



D To JK flip-flop conversion: Steps - Same as previous conversion

Hence, Available FF = D FF

Required FF = JK FF


Characteristic table of JK FF      Excitation table of D FF

$Q_n$	J	K	$Q_{n+1}$	D
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

$Q_n$	$Q_{n+1}$	D
0	0	D
0	1	1
1	0	0
1	1	1

$Q_n$	$Q_{n+1}$	00	01	11	10
0	0	0	0	1	1
1	1	1	0	0	1

$$D = Q_n \bar{K} + \bar{Q}_n J$$

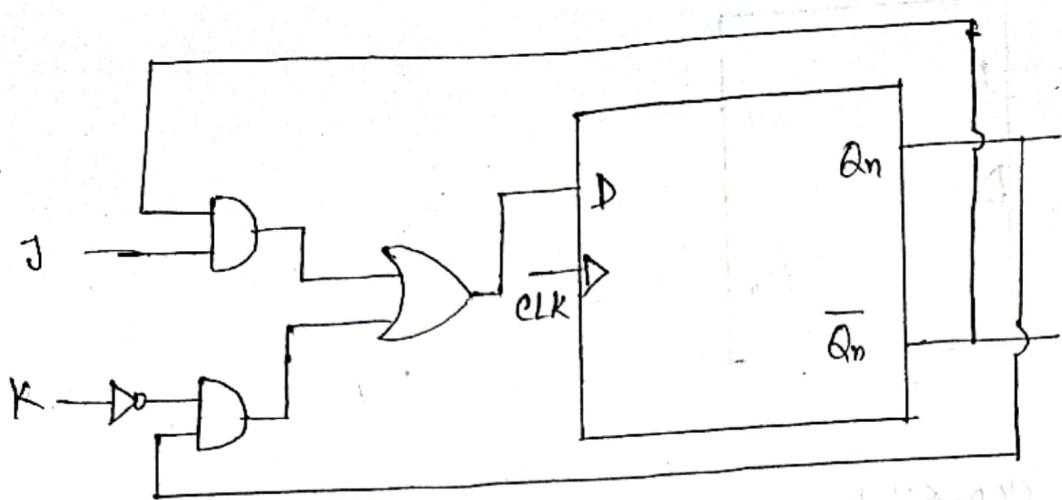

T to D flip flop conversion: Steps - Same as previous conversion

Here, Available FF = T FF


Required FF = D FF

Characteristic table of D FF

$Q_n$	D	$Q_{n+1}$	T
0	0	0	0
0	1	1	1
1	0	0	1
1	1	1	0


Excitation table of T FF

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

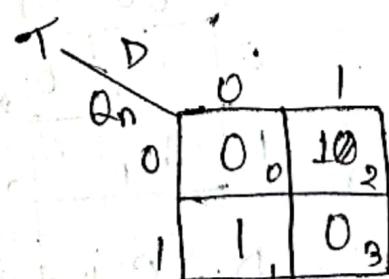

$$T = D \bar{Q}_n + \bar{D} Q_n$$

$$\Rightarrow D \oplus Q_n$$

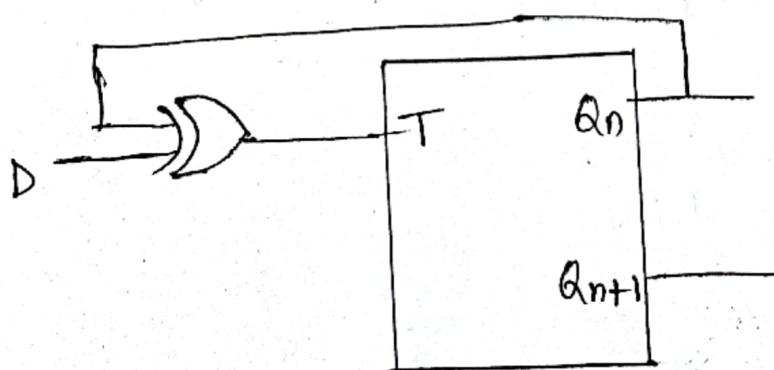

T to JK flip flop conversion: Steps - Same as previous conversion

Hence, Available FF = T FF

Required FF = JK FF

Characteristic table of JK FF


$Q_n$	J	K	$Q_{n+1}$	T
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1

Excitation table of T FF

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

$Q_n$	00	01	11	10
0	00	02	16	14
1	01	13	17	05

$$T = Q_n K + \bar{Q}_n J$$

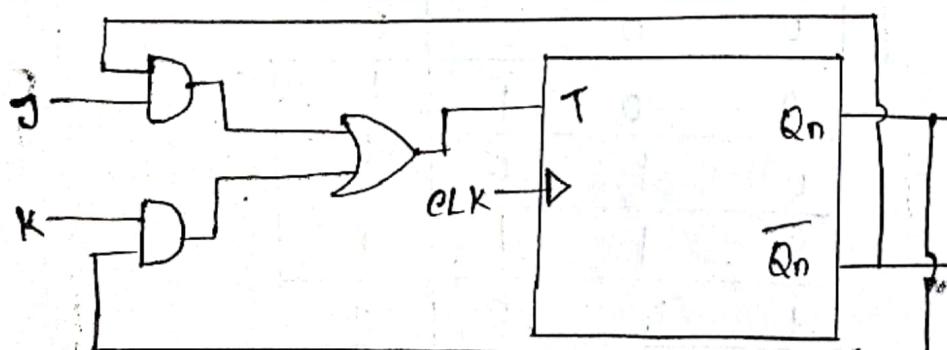

JK to SR, T to SR and D to SR Flip Flop conversion.

→ when  $S=1$  and  $R=1$  then  $Q_{n+1}$  = Invalid. But for JK, T and D,  $Q_{n+1} = J$  it will never go in Invalid state. So we cannot form JK to SR, T to SR and D to SR Flip Flop.

### Examples on Flip Flop

① A New FF is having behaviour as described below. It has two inputs  $X$  and  $Y$  and when both inputs are same and they are 1,1. The FF is going to set else FF resets. If both inputs are getting different and they are 0,1 the FF complements itself otherwise it is going to retain the last state which of the following expression is the characteristic expression of the new FF?

- (A)  $XQ + Y\bar{Q}$  (B)  $X\bar{Q} + YQ$  (C)  $X\bar{Q} + Y\bar{Q}$  (D) None  
(Truth table)

Inputs		
$X$	$Y$	$Q$
1	1	0
0	0	0
0	1	1
1	0	0
1	1	1

$Q_n$	$X$	$Y$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$Q_{n+1}$

$X$


$Q_n$

	00	01	11	10
0	0	1	1	0
1	0	0	1	1

$$Q_{n+1} = \overline{Q_n} + X + Q_n X$$

Ans A

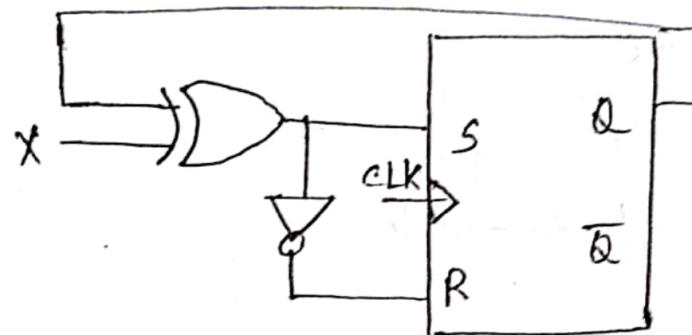- ② Make expression of  $Q^+$  for given circuit.



- A.  $XQ$
- B.  $X\bar{Q}$
- C.  $X \oplus Q$
- D.  $X \odot Q$

X	Q	$Q^+$
0	0	0
0	1	1
1	0	1
1	1	0

$$\begin{aligned} Q^+ &= \overline{X}Q + X\bar{Q} \\ &= X \oplus Q \end{aligned}$$